

Introduction to Computer Architecture

Chapter 4 - 1

The Processor

Hyungmin Cho

Department of Computer Science and Engineering
Sungkyunkwan University

Introduction

- **Micro-architecture** means the **internal** structure of a CPU
 - ❖ Externally, the CPUs of the same ISA has the same interface.
 - ❖ Internally, the CPUs can be composed different to each other, depending on their performance/efficiency targets

- Microarchitecture examples we will study
 - ❖ **Single-cycle**
 - Each instruction is executed in one cycle
 - It suffers from the long critical path delay, which limits the clock frequency
 - ❖ **Pipelined**
 - Execution is broken up into a series of steps
 - Multiple instructions are executed in an overlapped fashion.

Introduction

- Our example supports only a subset of RISC-V ISA
 - ❖ Arithmetic/logic: **add**, **sub**, **and**, **or**
 - ❖ Memory access: **lw**, **sw**
 - ❖ Control transfer: **beq**
- Covers most common operations of a typical RISC-style CPU

What Happens in CPU

- Load an instruction from (instruction) memory (***fetch***)
 - ❖ Memory address: PC
- Use the opcode field to identify the instruction type (***decode***)
 - ❖ Instruction[6:0] (i.e., lower 7 bits)
- These first two steps are identical for all instruction types.

What Happens in CPU

- Arithmetic/Logic instructions: **add**, **sub**, **and**, **or**
 - ❖ Read two operand values from the register file (*rs1*, *rs2*)
 - ❖ Perform calculation
 - ❖ Write the result back into the register file (*rd*)
 - ❖ Add 4 to PC

What Happens in CPU

■ Memory access: `lw`

- ❖ Read 1 word from the register file (*rs1*): base address
- ❖ Add the base address with the offset (*Immediate field*)
- ❖ Load word from data memory (Address: base address + offset)
- ❖ Write loaded word into the register file (*rd*)
- ❖ Add 4 to PC

What Happens in CPU

■ Memory access: **sw**

- ❖ Read 1 word from the register file (*rs1*): base address
- ❖ Add the base address with the offset (*Immediate field*)
- ❖ Read 1 word from the register file (*rs2*): value to store
- ❖ Store the word to data memory (Address: base address + offset)
- ❖ Add 4 to PC


What Happens in CPU

■ Control transfer: **beq**

- ❖ Read 2 words from the register file ($rs1$, $rs2$)
- ❖ Perform comparison (using ALU): Subtraction
- ❖ If $*rs1 == *rs2$
 - $PC \leftarrow PC + \text{immediate}$
- ❖ else
 - $PC \leftarrow PC + 4$


Single-cycle CPU Overview

- 1 cycle for all instructions (CPI = 1)

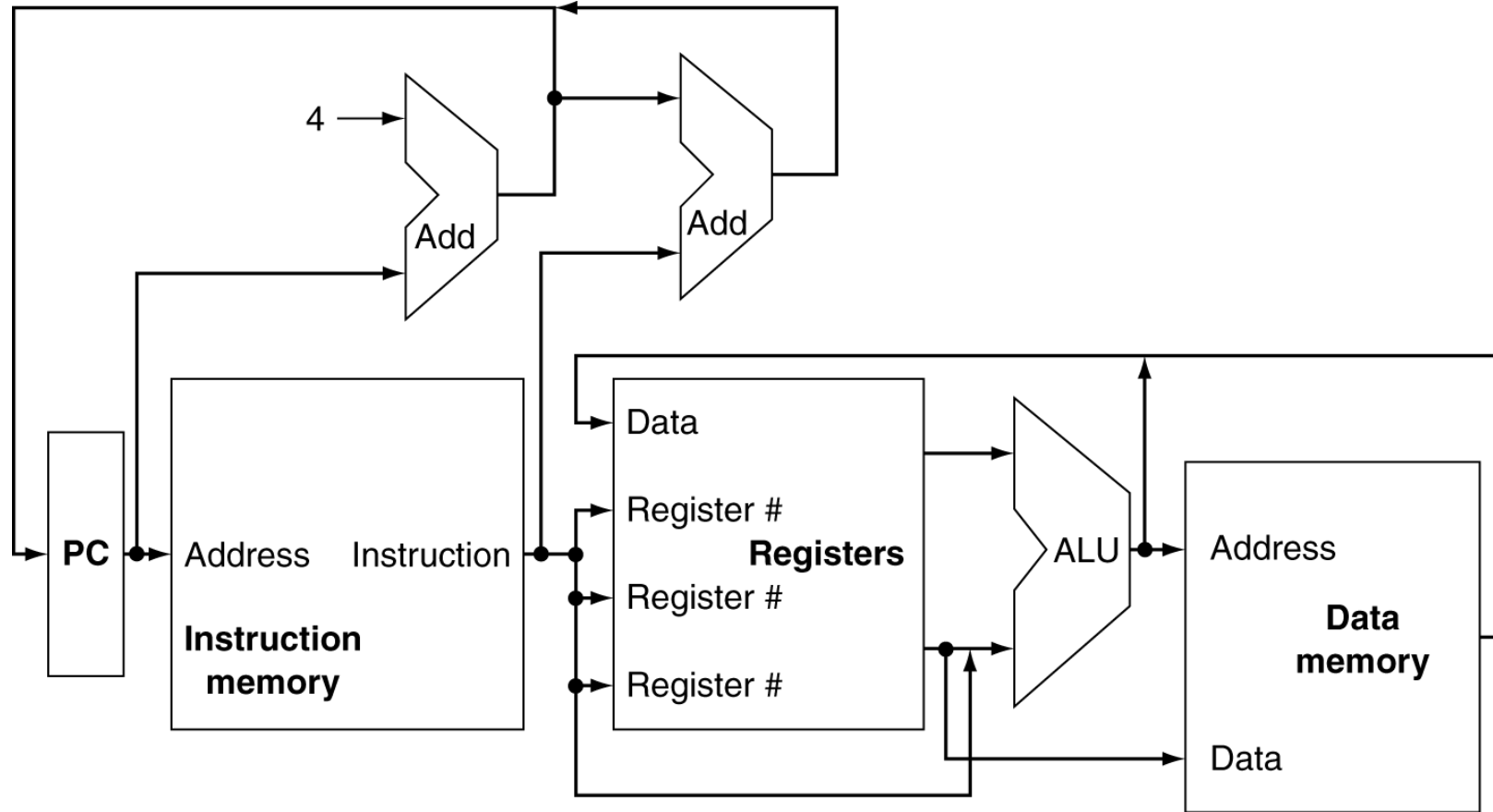

Instruction / Data Memory?

 - When describing a processor architecture in this lecture, we use separate units for instruction memory / data memory
- In reality, these are the same main memory.
- From the processor side, they may look like separate memory because we will use separate cache memory




Logic Design Basics: Combinational Logic

- Output is a function of the **current** input


- AND-gate

- ❖ $Y = A \& B$

 


- Multiplexer

- ❖ $Y = S ? I1 : I0$

 


- Adder

- ❖ $Y = A + B$

 

- Arithmetic/Logic Unit


- ❖ $Y = F(A, B)$

 

Logic Design Basics: Sequential Elements


■ Register: stores data

 - ❖ Uses a clock signal to determine when to update the stored value
- ❖ Edge-triggered: update when Clk changes from 0 to 1




Logic Design Basics: Sequential Elements

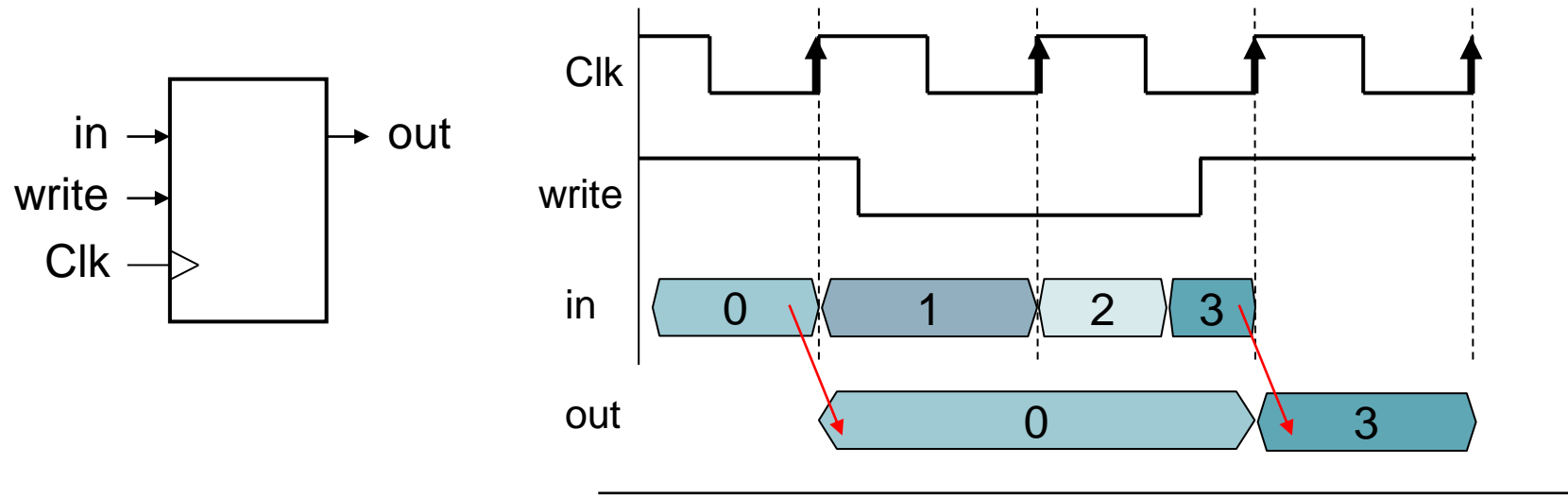- Register with write control
 - ❖ Only updates on clock edge when write control input is 1




Logic Design Basics: Wires

 
- Logic values (0/1) are delivered through wires



 
- If you need deliver multiple bits of data, need multiple wires



Simplified representation:

 


Logic Design Basics: Counters

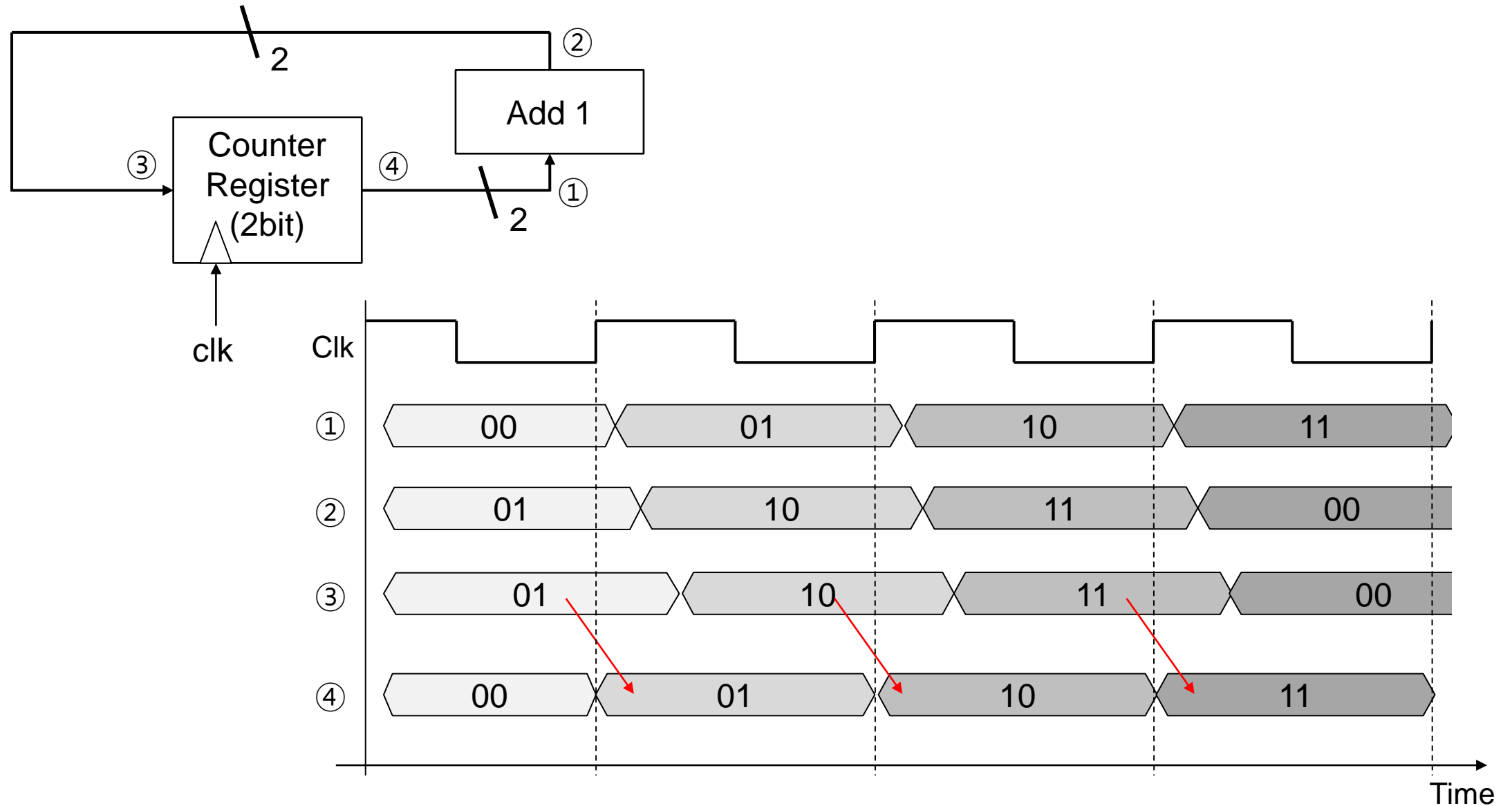


Instruction Fetch

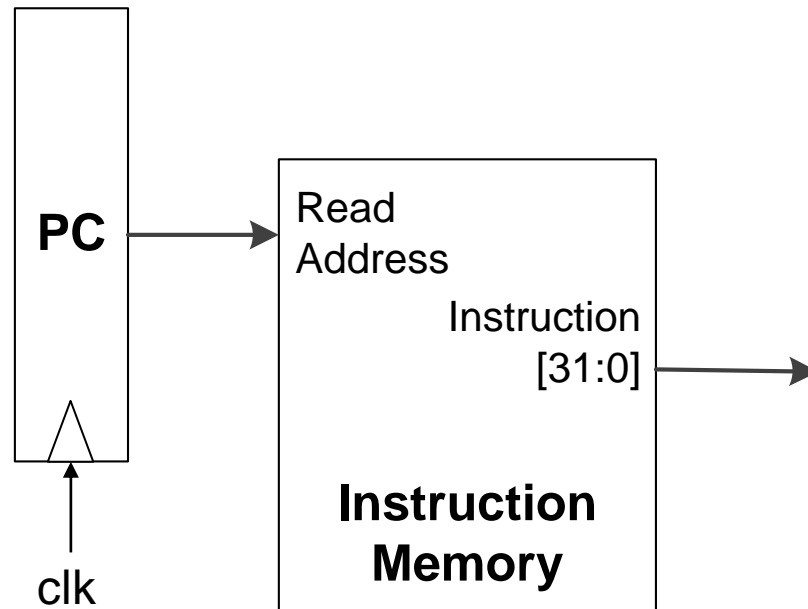- **PC: 32-bit register**
 - ❖ Remembers the current instruction address
- **Instruction Memory:**
 - ❖ For now, let's assume it behaves like a combinational logic i.e., it directly gives us the instruction at the PC address




Instruction Fetch

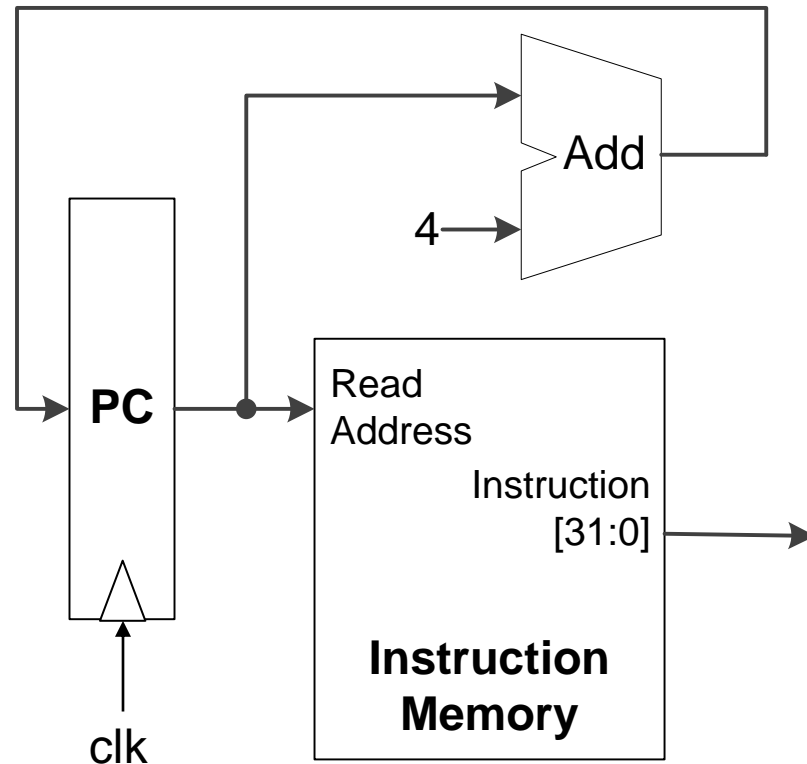- Advance to the next instruction
 - ❖ Next instruction is at $PC + 4$
 - ❖ In the next cycle (next clock period), PC should be changed to $PC + 4$



R-Format Instructions

 
- Read two register operands
- Perform arithmetic/logic operation
- Write the result into the destination register



- add → op: 0110011, funct3: 000 funct7: 0000000
- sub → op: 0110011, funct3: 000 funct7: 0100000
- and → op: 0110011, funct3: 111 funct7: 0000000
- ...


Register File

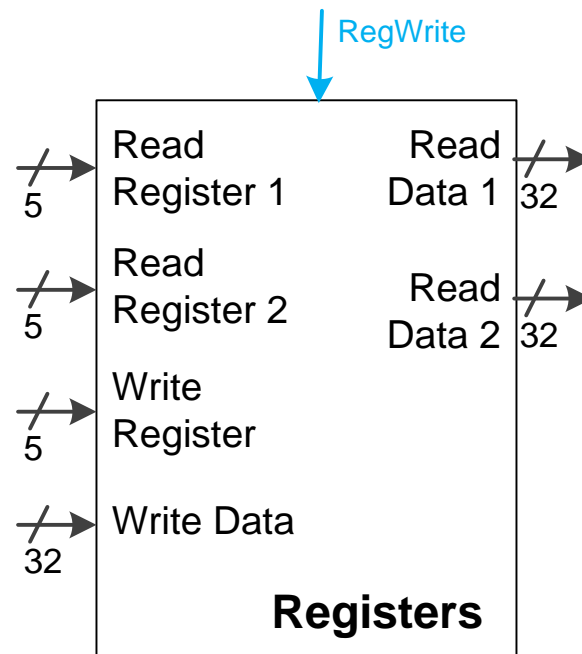- Read: Behaves like a combinational logic
 - ❖ Read Register 1 / 2: Register IDs from the current instruction
 - ❖ Read Data 1 / 2: The current value of the corresponding registers




Register File

 
- Write: Behaves like a sequential logic
 - ❖ If **RegWrite** is “1”, writes the value to the target register
 - ❖ Actual write happens when moving to the next cycle



Two Read Ports

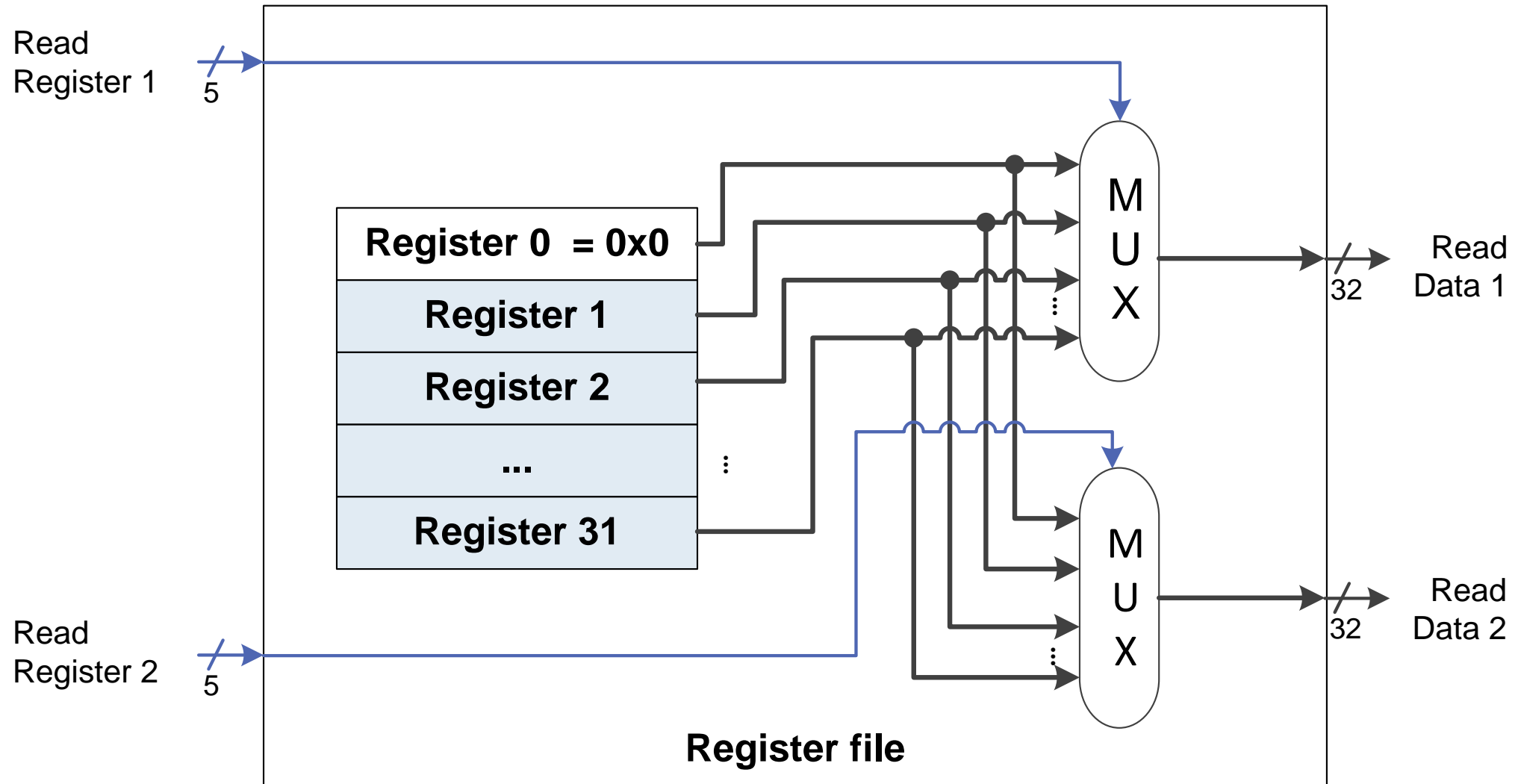


Write Port

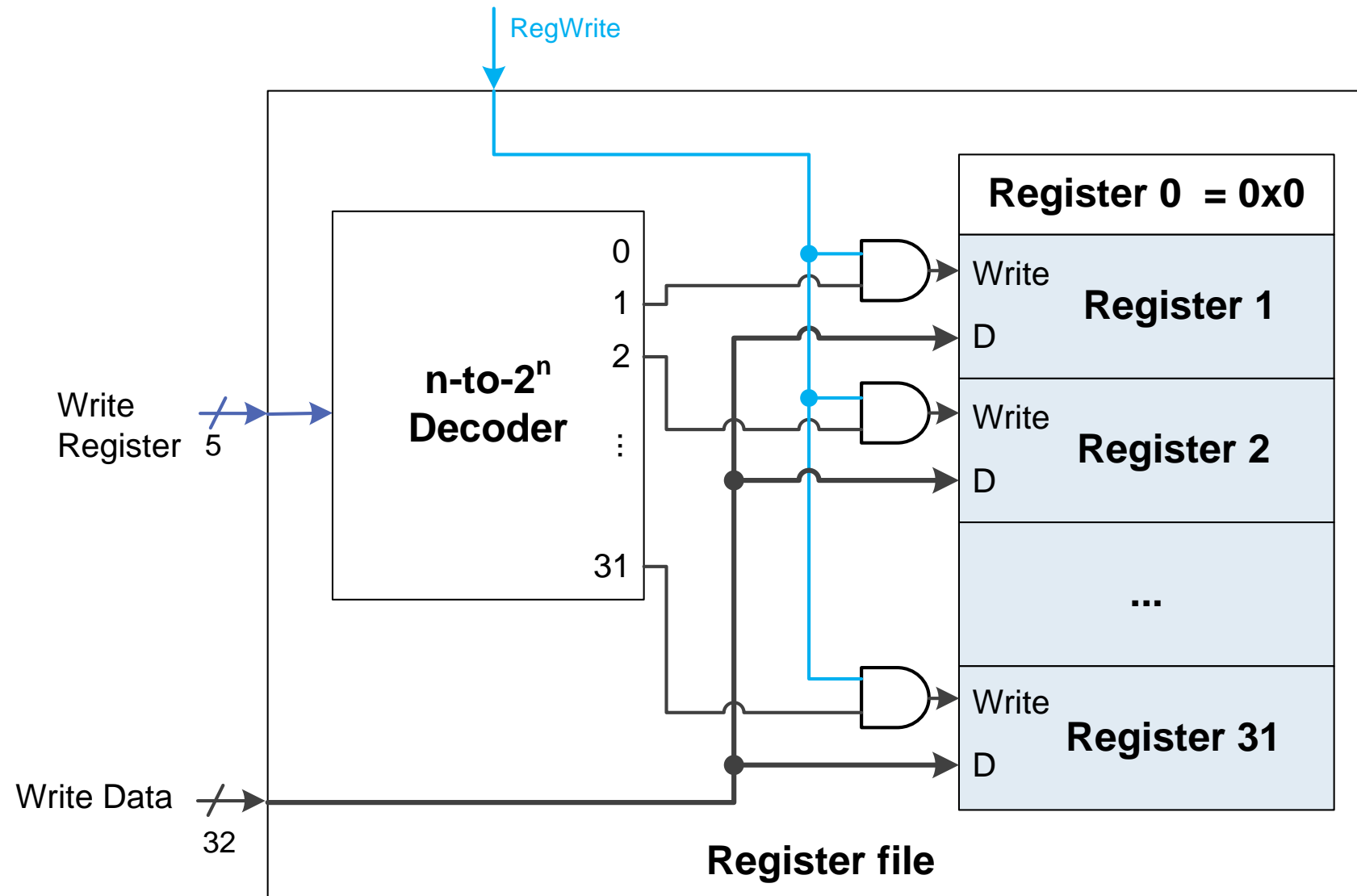

Arithmetic Logic Unit (ALU)

- Multiple functions

 - ❖ Add, subtract, shift, and, or, ...
- ❖ ALU operation (4-bit input) selects actual function



Arithmetic Logic Unit (ALU)

- ALU used for
 - ❖ Load/Store: Function = add
 - ❖ Branch: Function = subtract
 - ❖ R-type: Function is determined by the funct7 & funct3 fields


| ALU control lines | ALU Function |
|-------------------|--------------|
| 0000 | AND |
| 0001 | OR |
| 0010 | add |
| 0110 | subtract |
| ... | ... |
| ... | ... |

ALU Control Bits

| Opcode | ALUOp | Operation | Funct7 | Funct3 | ALU function | ALU control |
|--------|-------|-----------------|---------|--------|--------------|-------------|
| lw | 00 | load word | XXXXXXX | XXX | add | 0010 |
| sw | 00 | store word | XXXXXXX | XXX | add | 0010 |
| beq | 01 | branch if equal | XXXXXXX | XXX | subtract | 0110 |
| R-type | 10 | add | 0000000 | 000 | add | 0010 |
| | | sub | 0100000 | 000 | subtract | 0110 |
| | | and | 0000000 | 111 | AND | 0000 |
| | | or | 0000000 | 110 | OR | 0001 |


CPU for R-type Instructions

■ Datapath

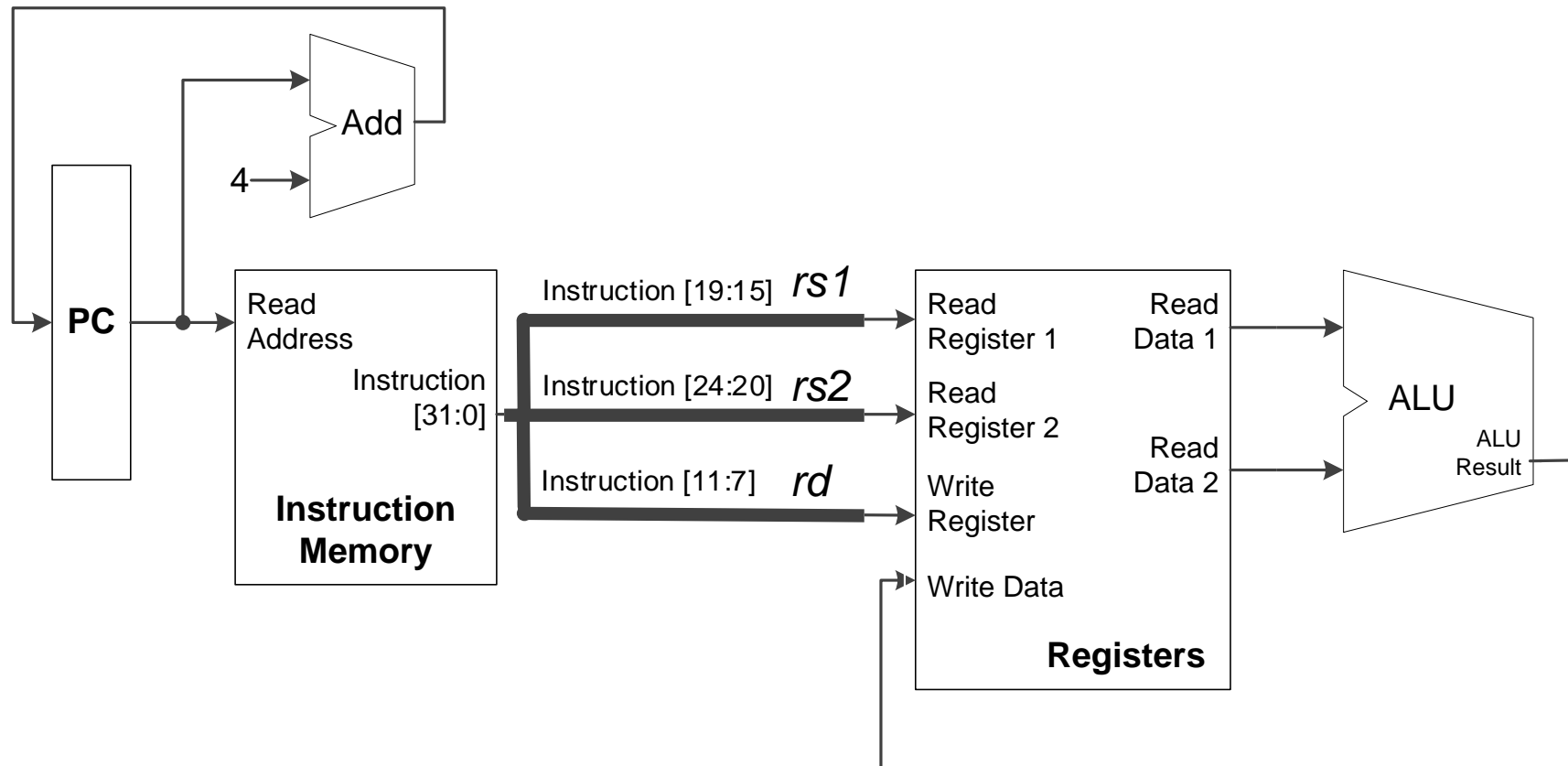


CPU for R-type Instructions

■ Datapath

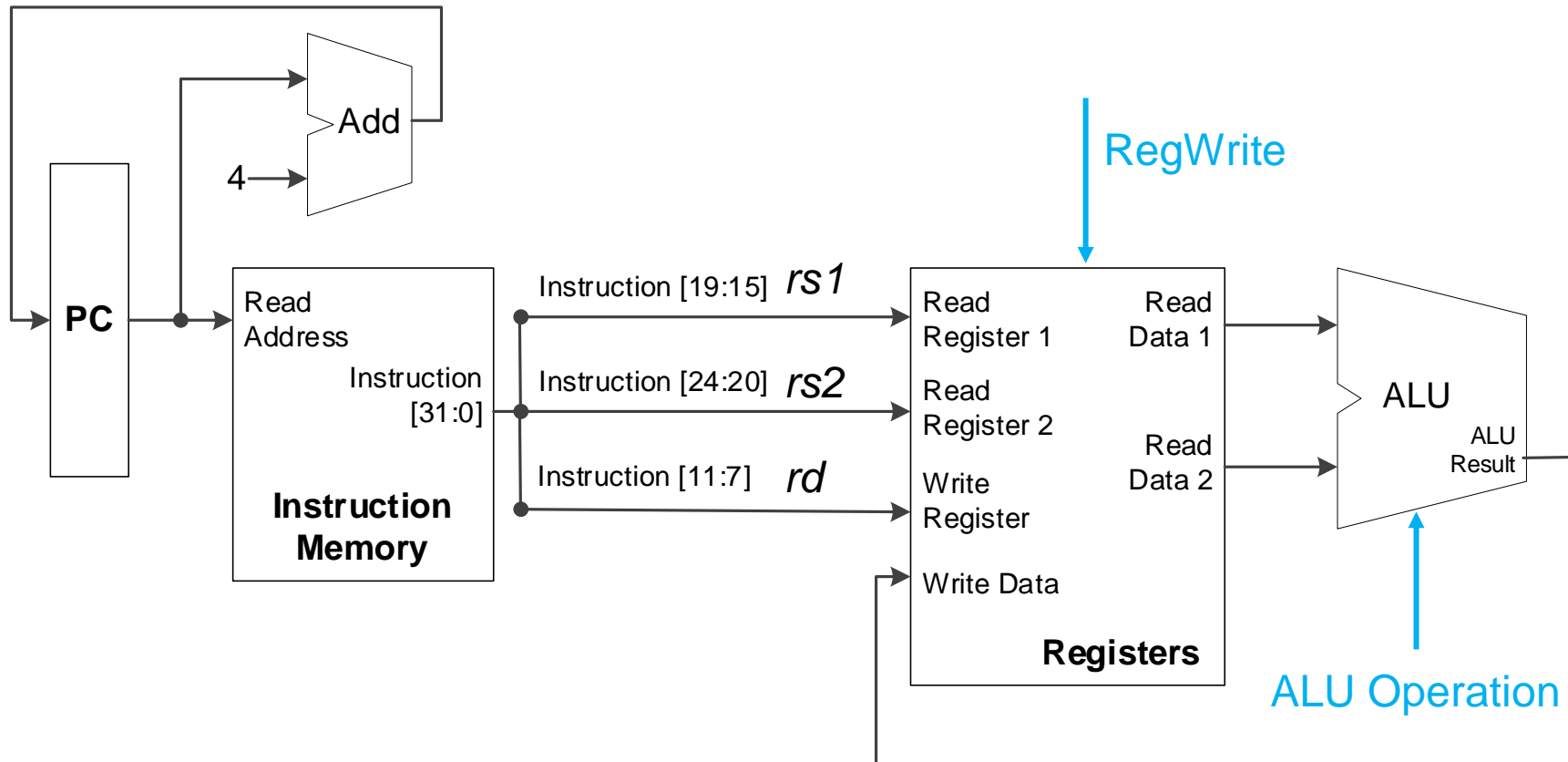


CPU for R-type Instructions

■ Datapath + Control signals

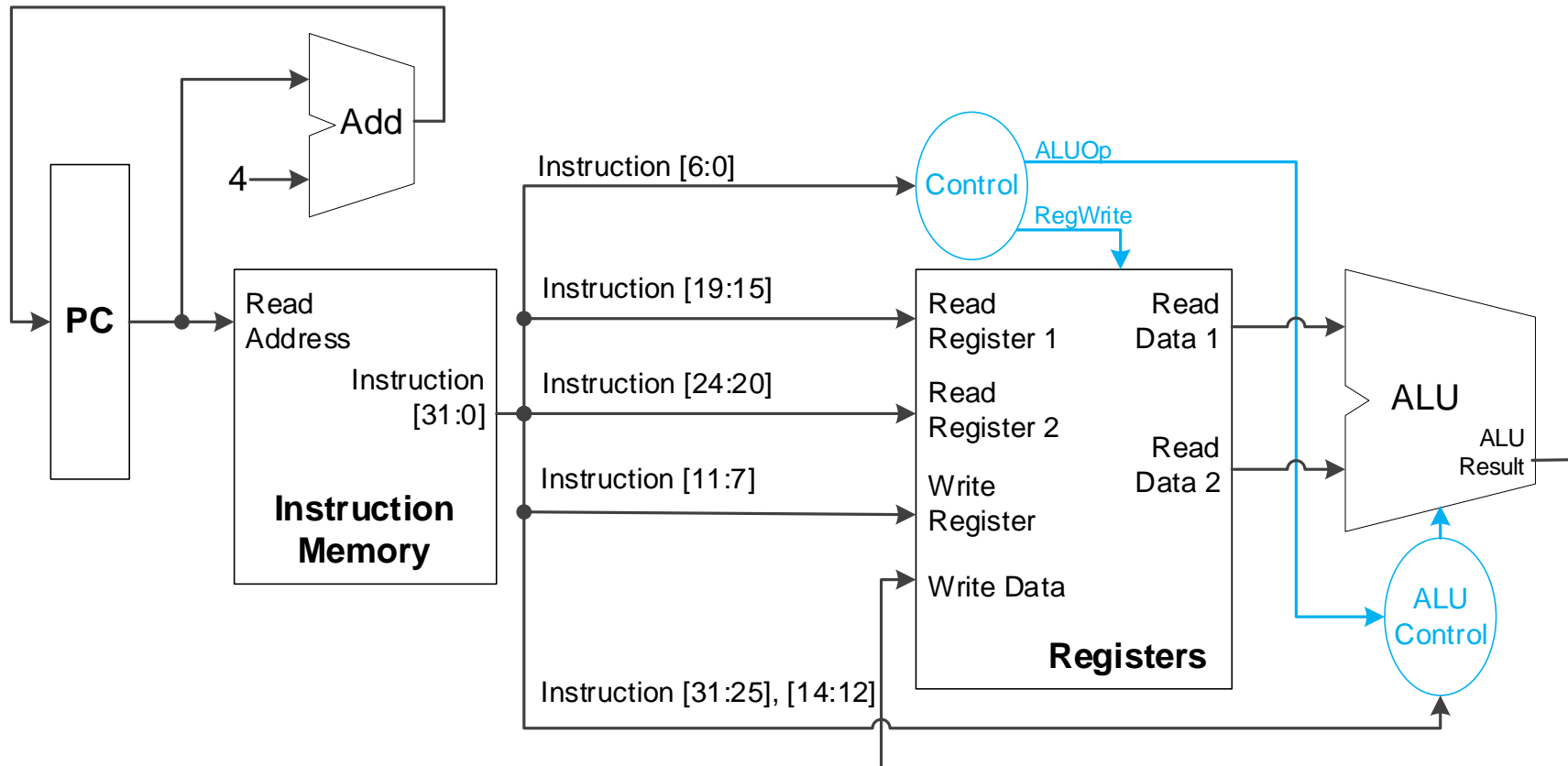


R-Type Execution Example

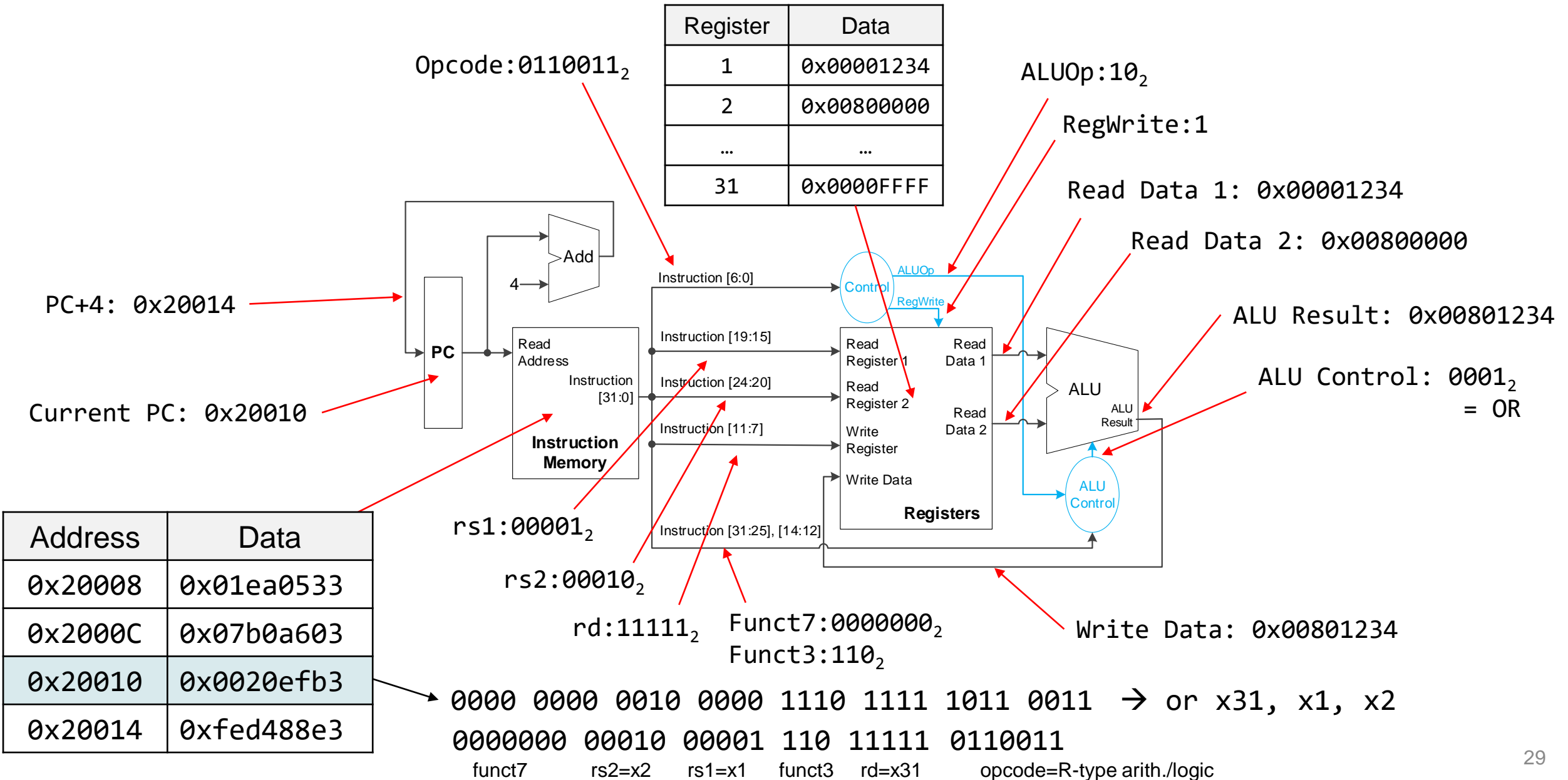


Load Instruction

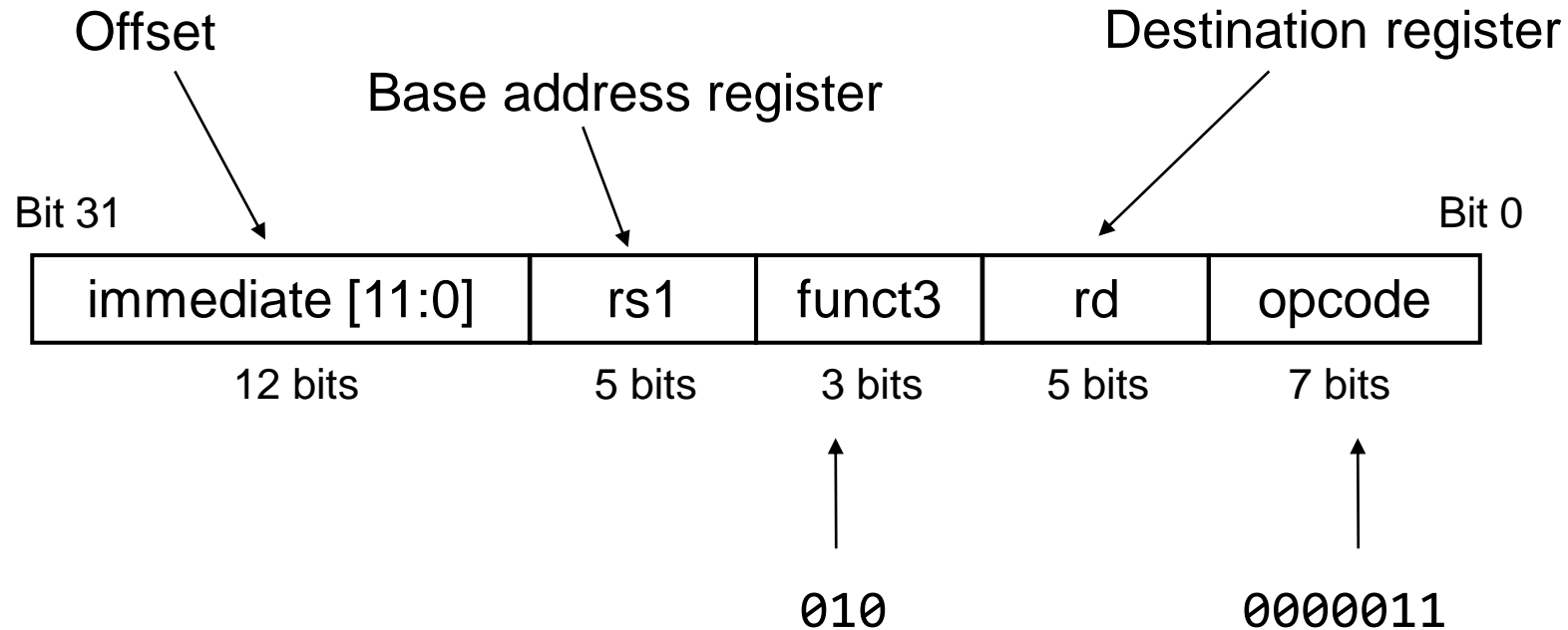- Address: Base address register + Offset




Store Instruction

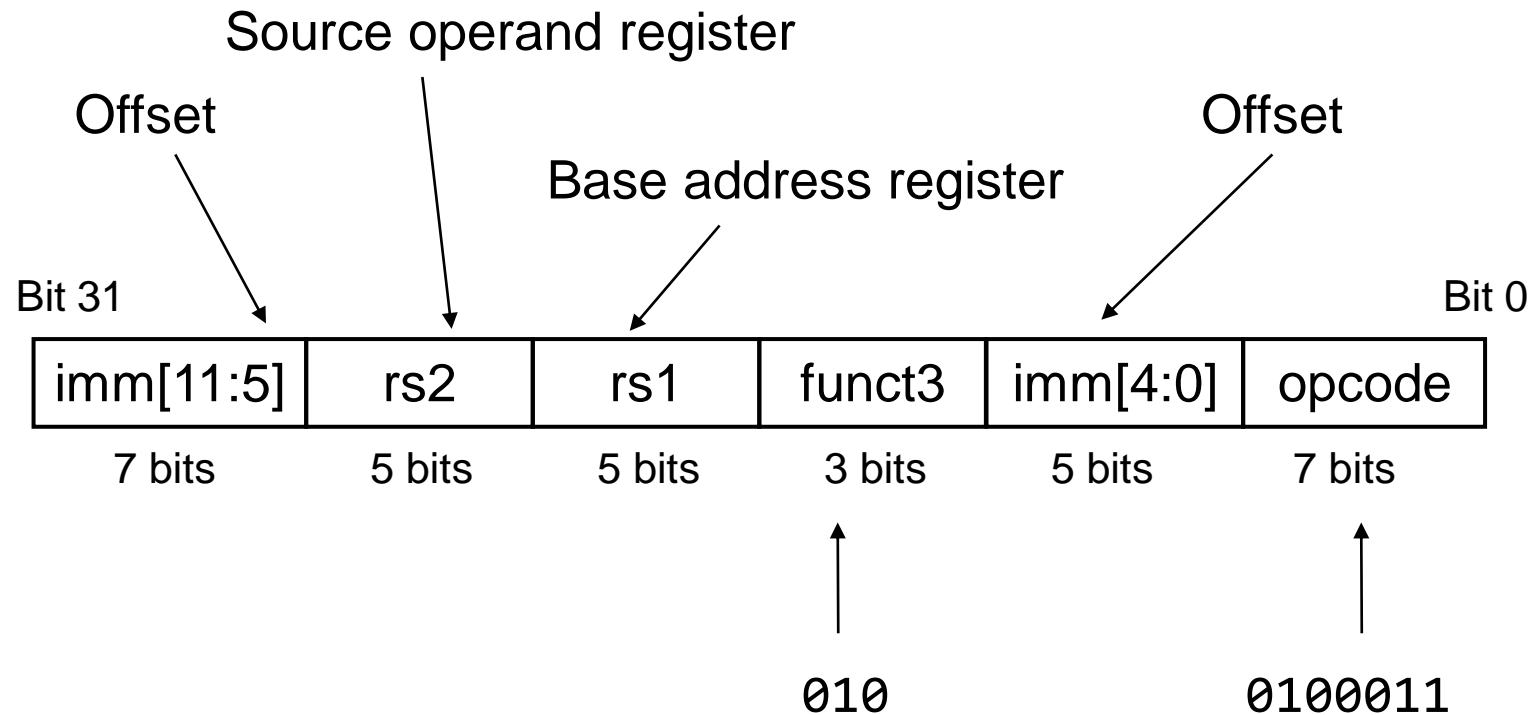- Address: Base address register + Offset



Data Memory

 - Read: Assume it behaves like a combinational logic
 - ❖ If **MemRead** is “1”, gives the current memory value from the address
- Write: Behaves like a sequential logic
 - ❖ If **MemWrite** is “1”, writes the data to the address




- Accessing main memory takes a long time
 - ❖ Typically, hundreds of cycles
 - ❖ Cache memory reduces the access time
- For now, we assume memory access does not add long latencies
 - ❖ i.e., assume we always have cache hit


Immediate Generation Unit (ImmGen)

- RISC-V instructions have immediate fields in various bit places
 - ❖ Can identify the format from the opcode
 - ❖ Sign-extend

| | | | | | | | | |
|-----------|------------------|-----------|-----|--------|------------|----------|--------|--------|
| I format | immediate [11:0] | | rs1 | funct3 | rd | opcode | | |
| S format | imm[11:5] | | rs2 | rs1 | funct3 | imm[4:0] | opcode | |
| SB format | 12 | imm[10:5] | rs2 | rs1 | funct3 | imm[4:1] | 11 | opcode |
| UJ format | 20 | imm[10:1] | | 11 | imm[19:12] | | rd | opcode |
| U format | imm[31:12] | | | | | rd | opcode | |

 

CPU for Load/Store

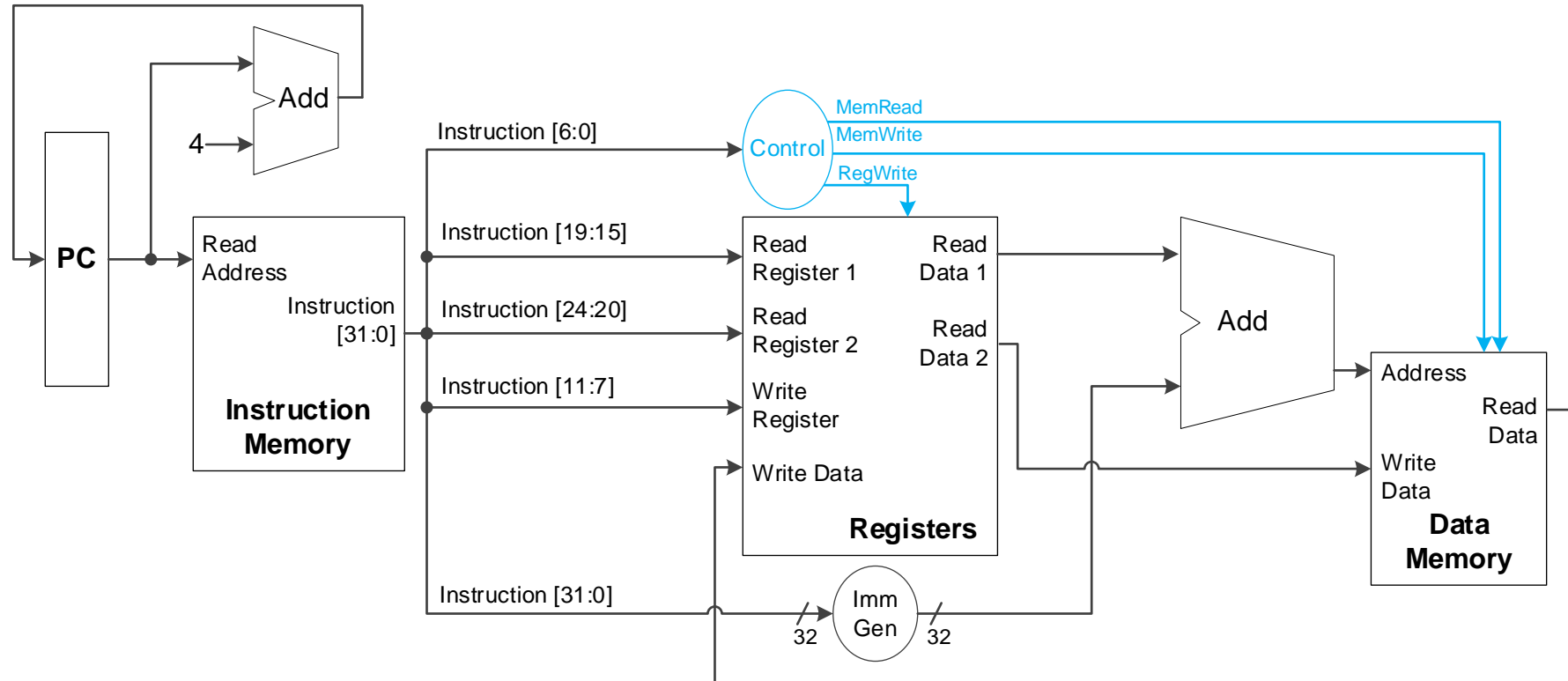

| | MemRead | MemWrite | RegWrite |
|-------|---------|----------|----------|
| Load | 1 | 0 | 1 |
| Store | 0 | 1 | 0 |

Store Execution Example

